
 


 
Step 4 . D:1 Output:0101(after posedge of CLK)




Step 5 . D:0 Output:1010(after posedge of CLK)



 
Step 6 . D:1 Output:0101(after posedge of CLK)



 Step 7 . D:1 Output:1011(after posedge of CLK)



 Step 8 . D:1 Output:0111(after posedge of CLK)



Step 9 . D:1 Output:1111(after posedge of CLK)

